

**Overview**

In this unit your students should:


- investigate the electrical behaviour of a NOT gate
- understand what a truth table shows
- find out how to use LEDs as indicators
- learn the truth tables and symbols of the six basic logic gates

This should not require more than 4 hours of class time.


Hour	Suggested Activity
1	<p>Launch them straight into the <b>Transfer characteristic of a NOT gate</b> practical. They will need access to the <b>Integrated Circuits</b> data sheet, and advice on keeping pin 1 at the bottom left-hand corner of the i.c.</p> <p>Discuss their answers to the first two questions of the <b>Combining Signals</b> exercises. Show students how to calculate a suitable value for the current-limiting resistor of an LED. Ask students to answer question 1 on page 15 of the text book before the next session.</p>
2	<p>Students should do the <b>Current-voltage graph for an LED</b> practical. Let them choose the colour of the LED that they are investigating.</p> <p>Discuss the simple model of an LED, and the use of the terms forward and reverse bias. Ask students to answer questions 3, 4 and 5 of the <b>Combining Signals</b> exercises before the next session.</p>
3	<p>Discuss their answers questions 3 to 5 of the <b>Combining Signals</b> exercises before setting them questions 6 and 7.</p> <p>As they finish the exercises, let them start the <b>Truth tables of logic gates</b> practical. They will be able to finish the practical next session.</p> <p>Ask students to answer questions 2 and 3 on page 15 of the text book before the next session.</p>
4	<p>Let the students finish off the practical from the last session.</p> <p>Use question 9 of the <b>Combining Signals</b> exercises to test their knowledge of logic gates. Set the remaining questions (4, 5 and 6) on pages 15 and 16 of the text book.</p> <p>Use a small informal test to probe their knowledge of logic gate truth tables and symbols. Ask students to finish any remaining questions and study <b>1.3</b> from the text book before the next session.</p>

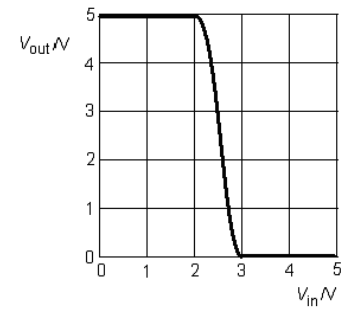**Model Answers**

- 1 A **1** is any signal which is between 3 V and 5 V and a **0** is any signal between 0 V and 2 V. This means that a 1 entering a NOT gate always results in a 0 at the output and vice versa.




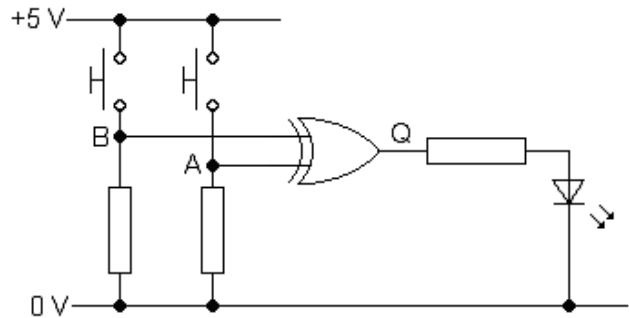- 2 Leave both switches alone, so that BA = 00. If the LED glows, Q is a 1, otherwise Q is a 0. Press the left-hand switch so that BA = 10 and use the LED to determine Q. Repeat for BA = 01 and 11 ...



- 3 (a) The LED voltage cannot exceed 2 V without the current rising to a large enough value to result in overheating. The resistor takes 3 V, limiting the current to a low enough value for the LED power to be below its maximum rated value.


(b)

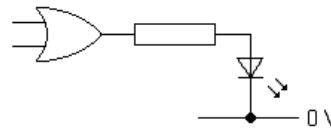

- (c)  $R = V/I = (5 - 1.9) / 2.2 \times 10^{-3} = 1.4 \times 10^3 \Omega$  or 1.4 k $\Omega$ .  
 $P = VI = (5 - 1.9) \times 2.2 \times 10^{-3} = 6.8 \times 10^{-3} \text{ W}$  or 7 mW, so 125 mW would be fine.

- 4 (a) Output only low when both inputs are high.

(b) NAND gate

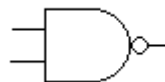

5

B	A	Q
0	0	1
0	1	0
1	1	0
1	0	0

- 6 (a) In forward bias, the anode is at a higher voltage than the cathode.  
 (b) There is no current in a reverse biased LED, so it does not glow. It's resistance is large. There is current in a forward biased diode when the voltage drop is 2 V, so it glows.

