

## Overview

In this unit your students should:

- learn about the transfer characteristics of an op-amp
- find out about the behaviour of silicon and zener diodes
- be able to analyse the behaviour of op-amp circuits
- know about ways of converting op-amp outputs into signals for logic gates

This should not require more than 6 hours of class time.

Hour	Suggested Activity
1	<p>Launch them straight into the <b>Op-amp transfer characteristic</b> practical.</p> <p>As they finish, get them to answer question 2 of the <b>Op-amps and Diodes</b> exercises.</p> <p>Introduce the silicon diode as a device which only lets charge flow one way through it. Show how it can be used with a voltage divider to convert the output of an op-amp into a signal which is high (1) or low (0), compatible with a logic gate.</p> <p>Ask them to answer question 1 on page 33 of the text book before the next session.</p>
2	<p>Students should do the <b>Transfer characteristic for a silicon diode</b> practical in this session.</p> <p>As students finish, they could answer questions 3 and 4 of the <b>Op-amps and Diodes</b> exercises.</p> <p>Ask them to answer question 2 on page 34 of the text book before the next session.</p>
3	<p>Launch them straight into the <b>Conversion to digital</b> practical.</p> <p>As students finish, they could answer question 5 of the <b>Op-amps and Diodes</b> exercises.</p> <p>Discuss their conclusions to the practical.</p> <p>Ask them to answer question 3 on page 34 of the text book before the next session.</p>
4	<p>Students could spend this session on the <b>Light sensor</b> practical. Step 7 is an extension activity which only a minority of students should attempt.</p> <p>Ask them to answer question 6 of the <b>Op-amps and Diodes</b> exercises before the next session.</p>
5	<p>Launch them straight into the <b>Transfer characteristic of a zener diode</b> practical.</p> <p>As students finish, they could answer question 7 of the <b>Op-amps and Diodes</b> exercises.</p> <p>Ask them to answer question 4 on page 34 of the text book before the next session.</p>
6	<p>Students who have managed to completely answer all four questions on page 34 should do the <b>Loading an op-amp</b> practical.</p> <p>Students who need to have another go at answering any of the exercises or questions could use this session for that, while their peers get on with the practical.</p> <p>Ask them to study <b>2.3</b> from the text book before the next session.</p>

**Model Answers**

1 (a) C is at +13 V when B has a higher voltage than A, otherwise C is at -13 V.

(b)  $R_{total} = 22 + 68 = 90 \text{ k}\Omega$

$I = V/R = 5 / 90 \times 10^3 = 5.6 \times 10^{-5} \text{ A}$

$V_B = IR = 5.6 \times 10^{-5} \times 68 \times 10^3 = 3.8 \text{ V}$

(c) Increasing the temperature of the thermistor reduces its resistance, raising the voltage at A. Once the voltage at A is above +3.8 V, the op-amp output C saturates at -13 V. The diode is now reverse biased, so there is no current in the resistors at the output, so they hold the output at 0 V.

(b)  $I = 10 \times 10 \text{ }\mu\text{A} = 100 \text{ }\mu\text{A}$


$R_{total} = V/I = (13 - 0.7) / 100 \times 10^{-6} = 1.2 \times 10^5 \text{ }\Omega$  or 120 k $\Omega$

$R_{bottom} = V/I = 4 / 100 \times 10^{-6} = 4 \times 10^4 \text{ }\Omega$  or 40 k $\Omega$


$R_{top} = 120 - 40 = 80 \text{ k}\Omega$

2 (a)

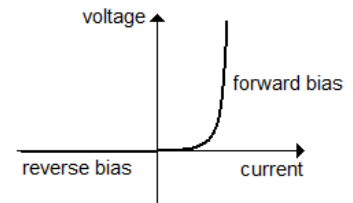(b) The current in a forward biased diode rises rapidly as the voltage goes above 0.7 V, so its resistance drops rapidly. In reverse bias there is no current, so the resistance is infinite.



(c)

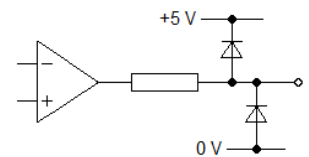

3 (a)


$R = V/I = (26 - 2) / 10 \times 10^{-3} = 2.4 \times 10^3 \text{ }\Omega$  or 2.4 k $\Omega$

(b)  $R_{total} = 20 + 10 + 30 = 60 \text{ k}\Omega$

$I = V/R = 15 / 60 \times 10^3 = 2.5 \times 10^{-4} \text{ A}$

$V_Z = IR = 2.5 \times 10^{-4} \times 30 \times 10^3 = 7.5 \text{ V}$

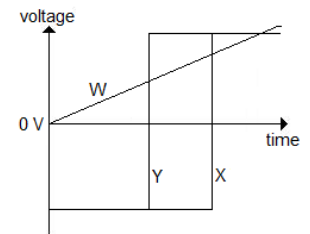$V_U = IR = 2.5 \times 10^{-4} \times (30 \times 10^3 + 10 \times 10^3) = 10 \text{ V}$



(c)

(d) When W is between 7.5 V and 10 V, Y is at +13 V and X is at -13 V, the LED is forward biased and the current in it allows it to glow. For other voltages at W, X and Y have the same voltage so there is no current in the LED.



4 (a)

(b)

(c)  $I = V/R = (15 - 5.1) / 220 = 4.5 \times 10^{-2} \text{ A}$

$P = VI = 5.1 \times 4.5 \times 10^{-2} = 0.23 \text{ W}$

230 mW is less than 500 mW

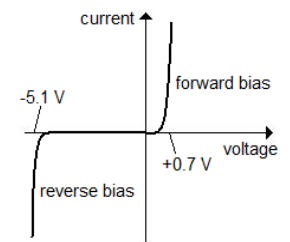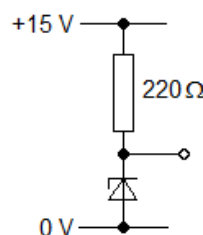

(d)

As the top rail moves up and down in voltage, the voltage across the zener diode hardly changes. For a voltage divider, the output is always a fixed fraction of the supply voltage, so variations in the supply voltage result in changes at the output.