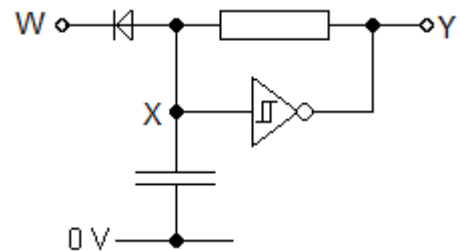


1 Link each **term** of a relaxation oscillator to its **meaning**.

term
period
enable
frequency
square wave
lower trip point
upper trip point

meaning
input signal required to make output go low
input signal required to make output go high
the time of for one cycle of the output signal
holding this high results in pulses at the output
a signal which alternates between high and low
the number of cycles of output signal per second

2 Complete the sentences for the relaxation oscillator shown opposite. Choose from these words.



- 0 V    0.7 V    2.2 V    2.8 V    5 V  
 capacitor    forward    resistor    reverse





When W is held low, the diode is in \_\_\_\_\_ bias. So X is at \_\_\_\_\_ and Y is at \_\_\_\_\_.

When W is held high, the diode is in \_\_\_\_\_ bias, allowing the \_\_\_\_\_ to charge up through the \_\_\_\_\_. When the voltage at X reaches \_\_\_\_\_, the voltage at Y drops to \_\_\_\_\_. This allows the \_\_\_\_\_ to discharge through the \_\_\_\_\_. The voltage at X falls until it reaches \_\_\_\_\_, at which point Y goes back to \_\_\_\_\_. This process continues while W is at \_\_\_\_\_, and Y goes straight to \_\_\_\_\_ as soon as W is taken to \_\_\_\_\_.

3 Complete the table for a relaxation oscillator.

<i>R</i>	<i>C</i>	<i>T</i>	<i>f</i>
22 kΩ	100 nF		
470 kΩ	33 μF		
100 kΩ		10 ms	
	270 μF	5 s	
27 kΩ			5 kHz
	10 μF		42 Hz

4 Complete the table for these oscilloscope traces. 0 V is halfway up the screen.

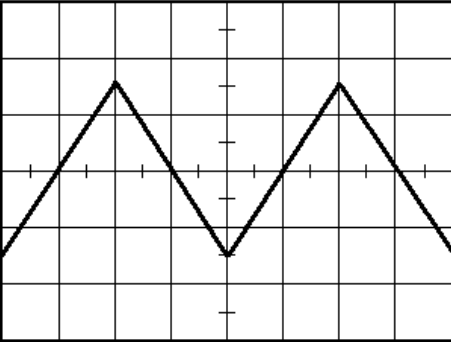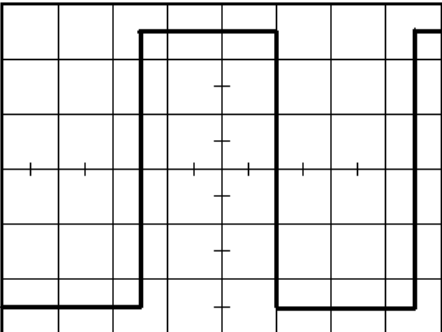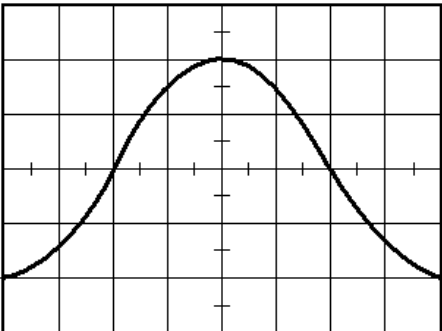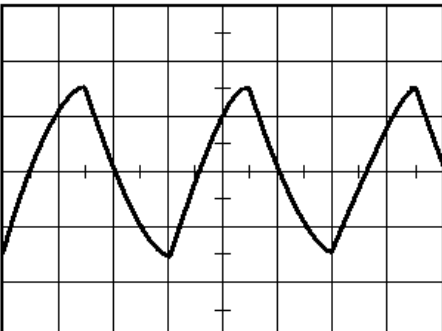screen trace	settings	amplitude	frequency
	<p>500 mV / div</p> <p>200 <math>\mu</math>s / div</p>		
	<p>2 V / div</p> <p>5 ms / div</p>		
	<p>10 mV / div</p> <p>50 <math>\mu</math>s / div</p>		
		<p>300 mV</p>	<p>170 Hz</p>