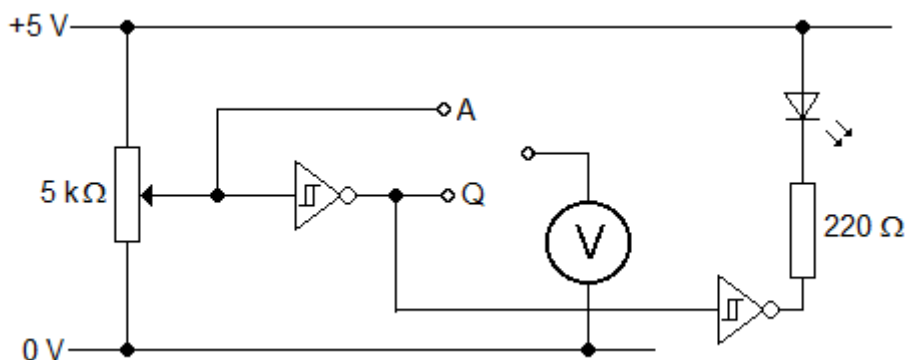



Schmitt trigger NOT gates

You are going to find the transfer characteristic of a Schmitt trigger NOT gate.

- 1 Assemble the circuit shown below. Note the use of a spare Schmitt trigger NOT gate to act as a driver.



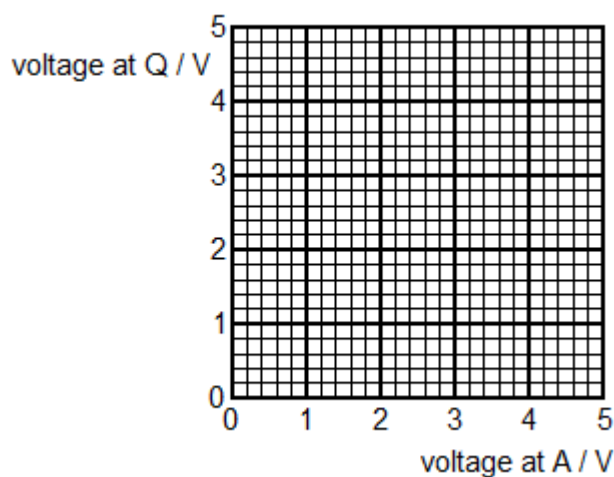- 2 Connect the voltmeter to A. Rotate the potentiometer. If all is well, the signal at Q should go low when A is high and vice versa.
- 3 Carefully determine the voltage at A required to make Q
 - fall from high to low
 - rise from low to high.
- 4 Use your observations to draw a graph on the axes below to show how Q changes as A is swept from 0 V to +5 V.




- 5 On the same axes, draw another graph to show the changes in Q as A is swept from +5 V to 0 V.

Relaxation Oscillator

You are going to assemble a relaxation oscillator and investigate its behaviour.

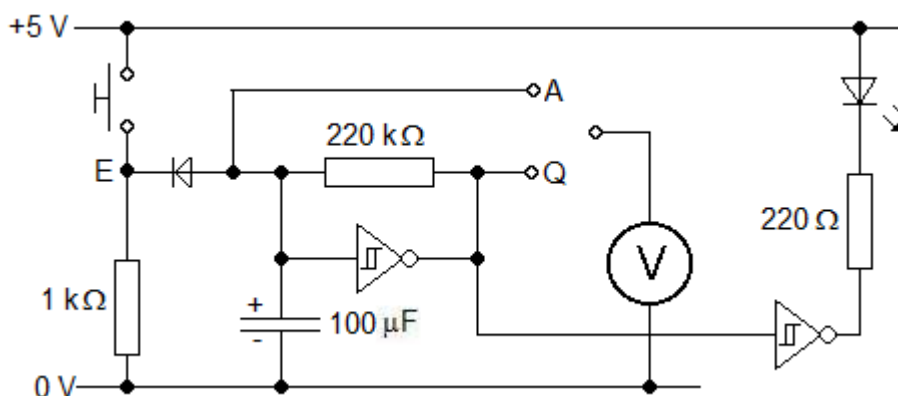- 1 Assemble the circuit shown below. Note the use of a spare Schmitt trigger NOT gate to act as a driver.



- 2 Press the switch. If all is well, the LED should go off and on at intervals of about 5 s.
- 3 Connect the voltmeter to A. Press the switch to raise E high. Verify that A shows the capacitor charging and discharging between the trip points of the Schmitt trigger NOT gate as Q swaps between high and low.
- 4 Verify that releasing the switch to make E low forces Q to go high immediately.
- 5 Use a stopwatch to time ten cycles of oscillation at Q. Hence obtain a value for the period T of the oscillator. Compare it with the value calculated from $0.5RC$.
- 6 Measure the values of T for the values of R and C given in the table below.


R	C	T	$0.5RC$
220 k Ω	100 μ F		11 s
100 k Ω	100 μ F		
47 k Ω	1000 μ F		
470 k Ω	10 μ F		

Fast oscillators


You are going to assemble a relaxation oscillator and investigate its behaviour with an oscilloscope.

- 1 Assemble the circuit opposite.
Use $R = 22\text{ k}\Omega$ and $C = 100\text{ nF}$.

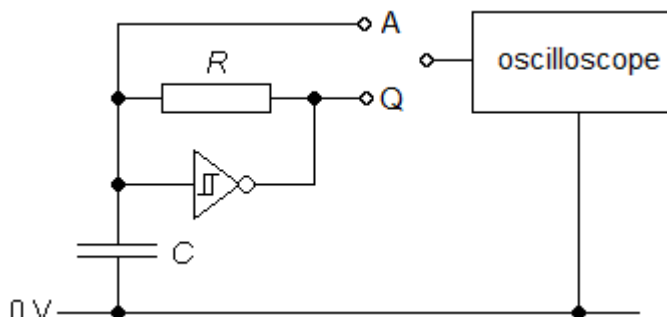- 2 Set the timebase and vertical amplifier of the oscilloscope to 0.2 ms/div and 1 V/div , with 0 V at the bottom of the screen.



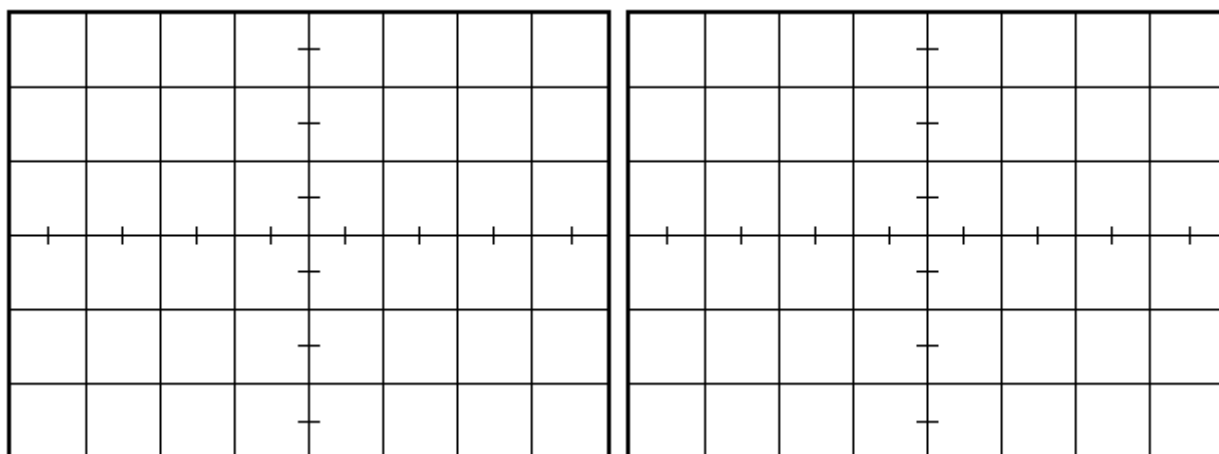- 3 Study the signals at A and Q. Sketch their traces on the screens drawn below.




- 3 Use the oscilloscope to measure the period T of the oscillator. Compare it with the value calculated from $0.5RC$.
- 4 Measure the values of T for the values of R and C given in the table below. Calculate a value for the frequency f of the oscillator from $f = 1/T$.

R	C	T	$0.5RC$	f
$22\text{ k}\Omega$	100 nF		1.1 ms	
$100\text{ k}\Omega$	100 nF			
$47\text{ k}\Omega$	10 nF			
$47\text{ k}\Omega$	1 nF			

Light-to-sound converter

You are going to assemble and test a system which has an interesting audible output.

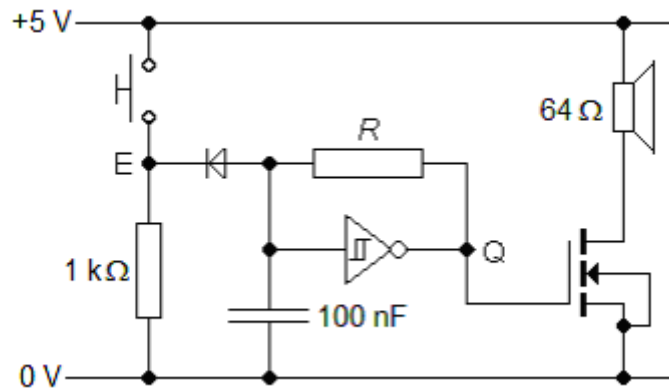- 1 Assemble the circuit shown below. Start with $R = 10\text{ k}\Omega$.



- 2 Use an oscilloscope to investigate the signal at Q when E is pulled high.
- 3 Investigate the effect of replacing the feedback resistor with an LDR.
- 4 Design and assemble a second oscillator which has a frequency of 1 Hz. Use its output to control the first oscillator.