

Overview

In this unit your students should:

- learn how to calculate voltage gain
- understand the meaning of the terms linear, gain and distortion for amplifiers
- meet an electret microphone

This should not require more than 3 hours of class time.

Hour	Suggested Activity
1	<p>Introduce the idea of voltage gain for an amplifier.</p> <p>Get students started on the Investigating a microphone practical.</p> <p>Ask students to study 6.1 from the text book before the next session.</p>
2	<p>Require students to answer all of the questions of the Amplifiers exercises.</p> <p>As they finish, let them start the Voltage gain practical. Only a minority of candidates are likely to get beyond step 2 in the time available.</p> <p>Ask students to answer question 1 on page 97 of the text book before the next session.</p>
3	<p>Let students finish the Voltage gain practical.</p> <p>As they finish, let them answer question 2 on page 97 of the text book.</p> <p>Ask students to study 6.2 from the text book before the next session.</p>

Model Answers


1 (a) An amplifier increases the amplitude of an a.c. signal without altering its shape.

(b) $V_{\text{out}} = GV_{\text{in}} = 6 \times 0.5 = 3.0 \text{ V}$. The frequency is unchanged at 340 Hz.

(c)

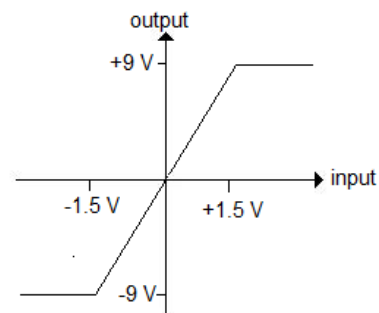(d) An input of 1.5 V results in an output of $6 \times 1.5 = 9 \text{ V}$.

Since the output voltage cannot go higher than the top supply rail voltage, input signals above 1.5 V result in a 9 V output. So signals with amplitudes above 1.5 V will be distorted at the output, with the top and bottom of their waveforms flattened.



2 (a) The circuit transfers information about sound waves into a.c. signals.

(b) $V = IR = 20 \times 10^{-6} \times 5 \times 10^3 = 1.0 \times 10^{-1} \text{ V}$ or 100 mV

(c) The capacitor blocks the 6 V bias voltage across the microphone, but allows the a.c. signal across the resistor to get to the output.

(d) $T = 1/f = 1/2.5 \times 10^3 = 4.0 \times 10^{-4} \text{ s}$

