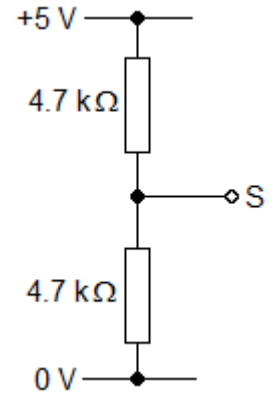


Loading a voltage divider


You are going to investigate the effect of drawing current from a signal source.

1

- 1 Assemble this voltage divider circuit on your breadboard.
The signal at S should be a fixed +2.5 V.




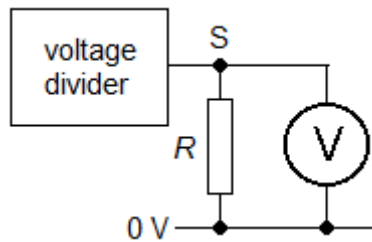- 2 Draw current from S with a load resistor R , as shown below.
Start off with $R = 220 \Omega$. Record the voltage at S (about 0.25 V).




- 3 Repeat step 2 for the other values of load resistor shown in the table.

load	output
220 Ω	
2.2 k Ω	
22 k Ω	
220 k Ω	
2.2 M Ω	

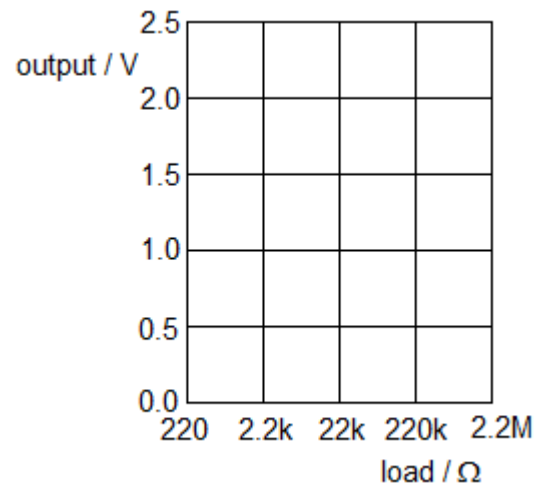

- 4 Plot your measurements on the axes shown. Note the use of a **log scale** to accommodate the large range of values on the horizontal axis. Join up the points and label the line **S**.

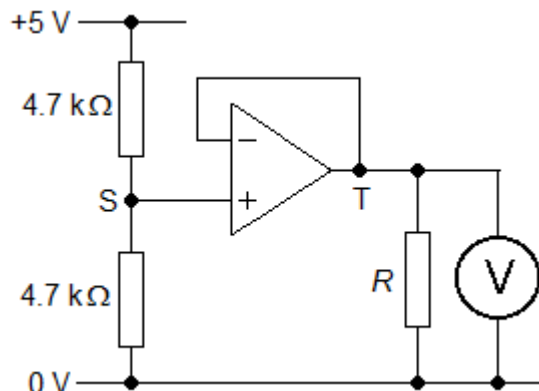- 5 Now insert an op-amp voltage follower between the voltage divider and the load. Record the voltage at T for the values of R in the table above.




- 6 Plot the measurements on the axes above. Join up the points and label the line **T**.


Transfer characteristic of a voltage follower

You are going to find out how the output voltage of a voltage follower is related to its input voltage.

- 1 Assemble this circuit.

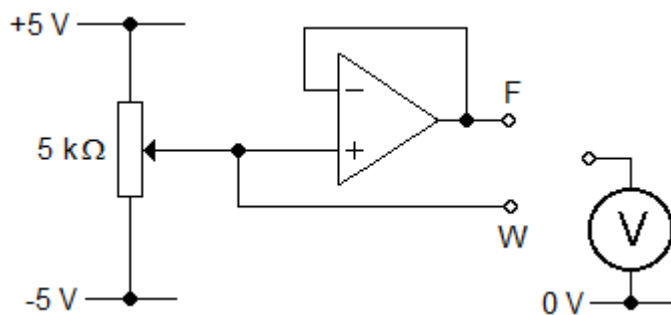

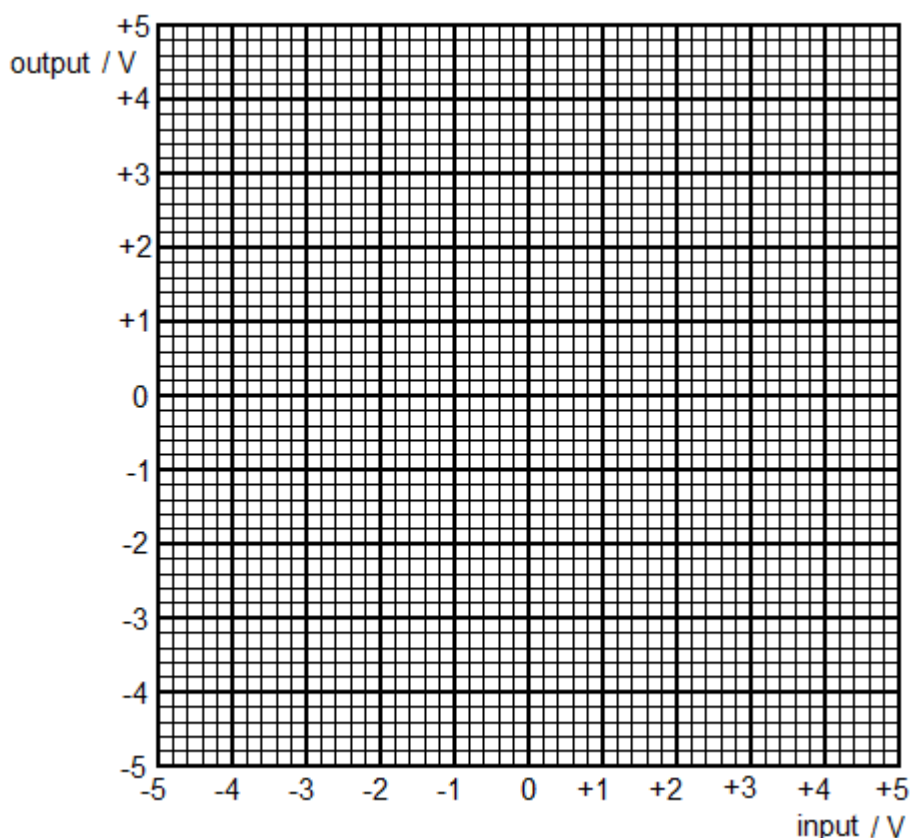- 2 Connect the voltmeter to W. Check that the voltage at the input of the voltage follower V_{in} can be varied from +5 V to -5 V.
- 3 Set V_{in} to +5.0 V. Measure the voltage at F, V_{out} . Use these values of V_{in} and V_{out} to plot a point on these graph axes.



- 4 Reduce the voltage at V_{in} by 0.5 V, measure V_{out} and plot another point on the graph.
- 5 Repeat step 4 until V_{in} reaches -3.5 V. Join the points with two straight lines, one for the linear region and another for the saturation region. Label the two regions.